
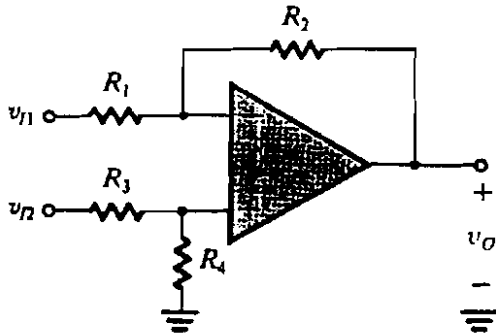


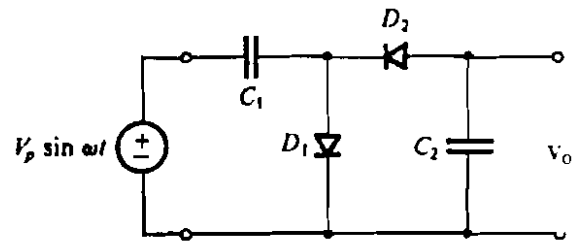1. Give a circuit shown as follow, where v_o is the output voltage and v_1 and v_2 are input voltage. [20]




Please answer the following questions:


- What is the input resistance seen by v_1 alone? (by setting to v_2 to zero)
 - What is the input resistance seen by v_2 alone? (by setting to v_1 to zero)
 - Give the output voltage v_o with respect to the resistors R_1 , R_2 , R_3 , R_4 and input v_1 and v_2 .
 - If the output is proportional to the voltage difference ($v_1 - v_2$), then this circuit is called as OP difference amplifier. Please give the relationships between R_1 , R_2 , R_3 and R_4 which can make this circuit.
2. Give a circuit, shown as follow, composed of two sections in cascade: a clamp formed by C_1 and D_1 , and a peak rectifier formed by D_2 and C_2 . When the circuit is excited by a sinusoid of amplitude V_p , the clamping section provides the voltage waveform of output v_o . Please the output voltage v_o and draw it. Note that this circuit is commonly called by voltage doubler. [15]



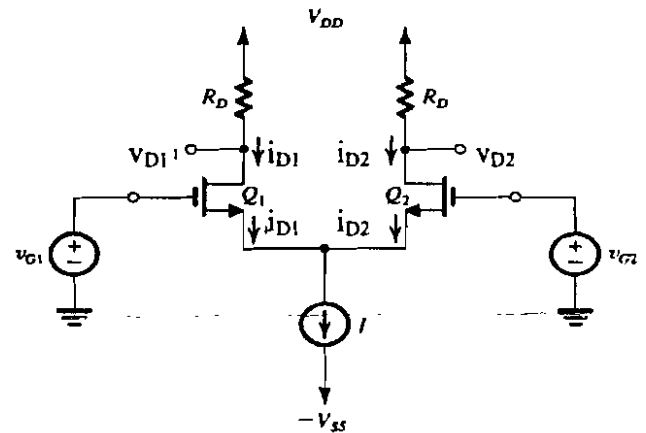3. Give a basic MOS differential-pair circuit, shown as follow. It consists two matched transistors Q_1 and Q_2 , whose sources and joined together and biased by a constant-current source I . Please derive the voltage of v_{D1} and v_{D2} . [15]



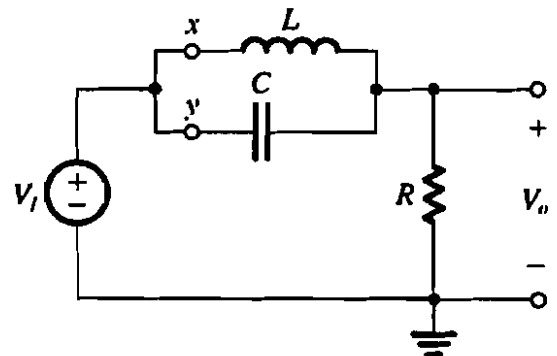4. Give a "Notch" filter, shown as follow. The natural frequency is $\omega_0 = \sqrt{LC}$. [15]




- a. Please show the transfer function.

$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s^2 + \omega_0^2)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$


- b. Please give the value of a.

- c. Please show the value of Q.

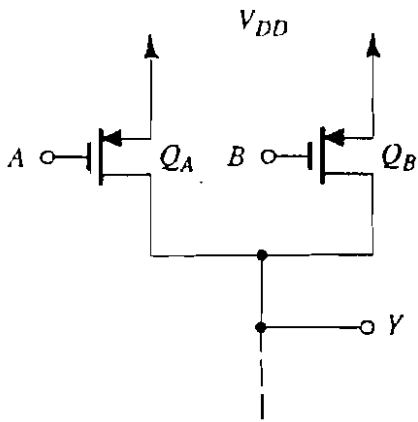
5. Give three pull-down CMOS gates circuits, please try to analyze these circuits and give their Boolean expression with respect to inputs and output. [15]



(a)

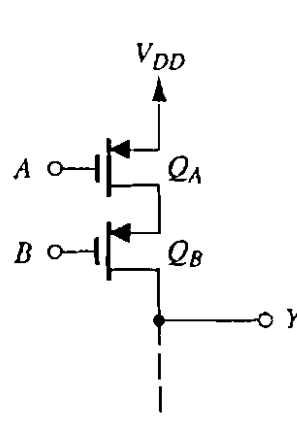

(b)

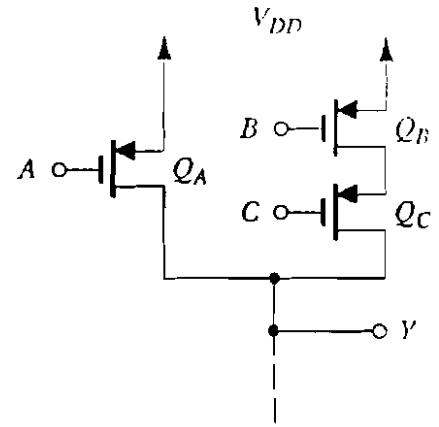

(c)

6. The α is called as common-base current gain. And the β as common-emitter current gain. Please answer the following questions: [20]
- The relationship between i_E , i_C and i_B .
 - The relationship between i_E and i_C with respect to α .
 - The relationship between i_E and i_C with respect to β .
 - The relationship between α and β .

