
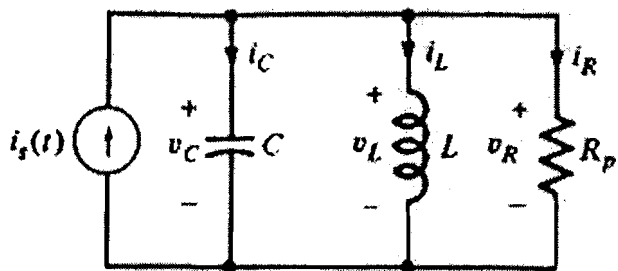


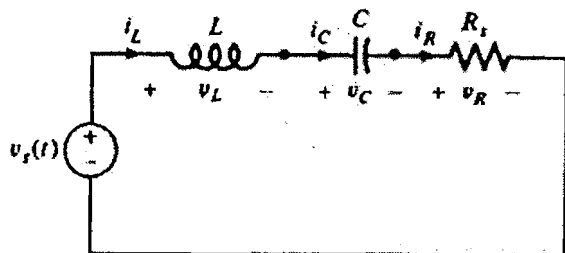1. Please describe the theorem of KCL and KVL and Ohm's Law. [10 credits]
2. Please explain the theorem of superposition of electronic circuit. [10 credits]
3. Please give the impedance of capacitor and inductor. [10 credits]
4. Give the following two linear time-invariant circuits, shown as follows. Please write down their standard forms of second-order differential equations with respect to the input source of given circuit. [10]



(a)




(b)

5. Give an ideal transformer, shown as follow. Please give the definition of the following: [15 credits]

A relationship is given as

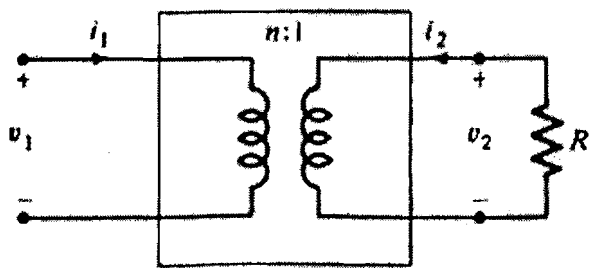- A. $v_1/i_1 = (?)$
- B. $(v_2/i_2) = (?)R$.


Please write down the answers of part (A) and (B).



6. Give a ladder circuit shown on the following figure. The input terminal is a voltage v and output terminal is voltage v_4 . There are total 4 resistors $R_1, R_2, R_3,$ and R_4 (where $R_1=R_2=R_3=R_4 = 10\Omega$) and the input voltage $v=10$ (V). Please answer the following questions: [15

credits]

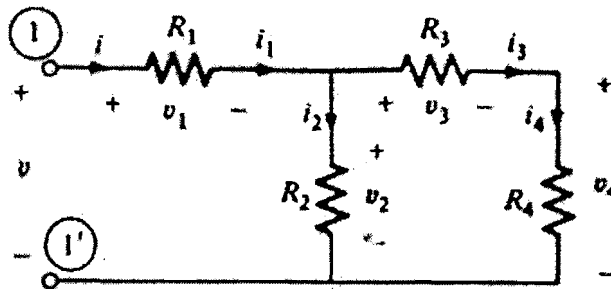- a. Please give the value of voltage, v_2 [5]
- b. Please give the value current, i_1 [5]
- c. The equivalent resistance R of all resistors. [5]




7. Give the following circuit, shown as follow. Please answer the following questions:

$$i_1 = (A) v_1 - (B) v_2$$

$$i_2 = (C) v_1 + (D) v_2$$

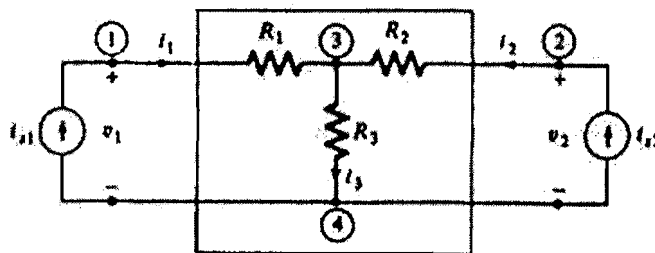, where the resistors $R_1, R_2,$ and R_3 are all equal to 10Ω and the current source i_{s1} is 1 Ampere and the current source i_{s2} is 1 Ampere. Please write down the answer of part (A), (B), (C), and (D) with respect to the given values of resistors and current sources. [15 credits]



8. Give a RC circuit, shown as follow. Please use the general conditions of capacitor: $v_c(t_0)=0, t_0=0,$ and $v_{oc}(t) = E, t \geq 0$. Please give the voltage of $v_c(t)$ corresponding to the given circuit and general conditions of capacitor. [15 credits]

